


Problem of the week

Current and circuits


(a) X and Y are two cylindrical wires. X has resistivity ρ , radius r and length L . Y has resistivity 2ρ , radius $2r$ and length $2L$. Determine the ratio $\frac{R_X}{R_Y}$ of the resistance of X to that of Y.

(b) Each of the four resistors in circuits (i) and (ii) has resistance $20\ \Omega$. Calculate the resistance between X and Y in each case.


(i)

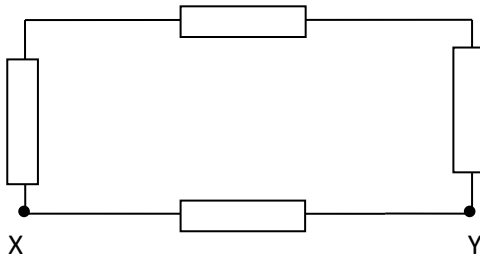

(ii)

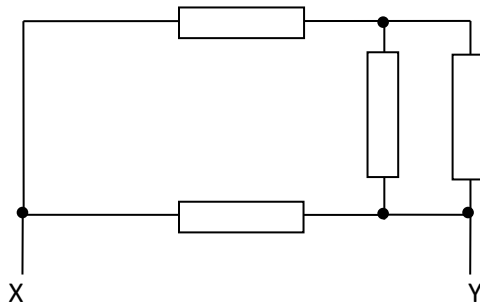

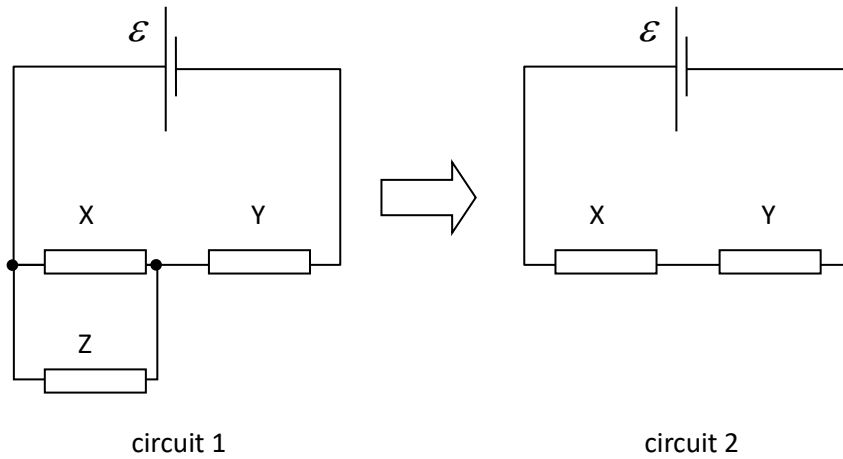
(c) In circuit 1, X, Y and Z are identical resistors of constant resistance. When resistor Z burns out the circuit becomes circuit 2.



Determine the ratios

- (i) $\frac{P_{X1}}{P_{X2}}$ of the power dissipated in resistor X in circuit 1 to the power in X in circuit 2,
- (ii) $\frac{P_{Y1}}{P_{Y2}}$ of the power dissipated in resistor Y in circuit 1 to the power in Y in circuit 2.

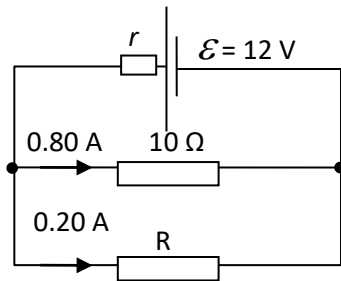
(d) In the circuit shown the cell has emf $\mathcal{E} = 12 \text{ V}$ and internal resistance r .




Calculate

- (i) R ,
- (ii) r .

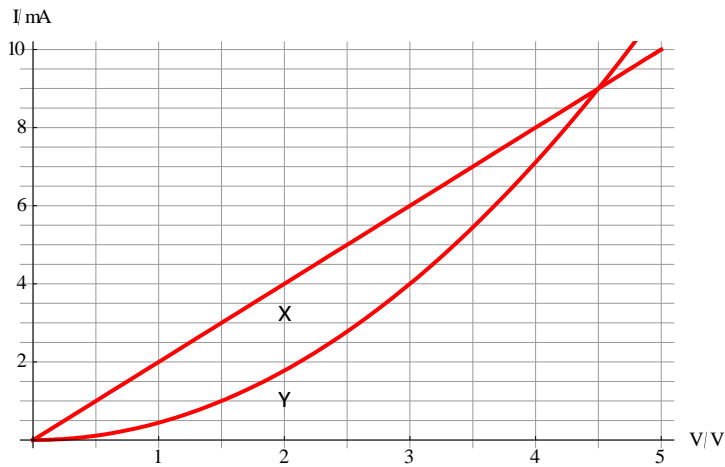(e) The graph shows the I-V characteristics of two resistors X and Y.



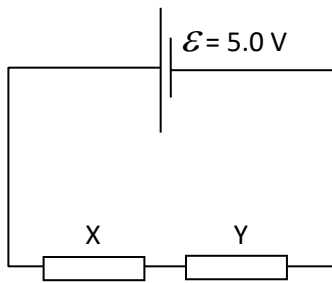X and Y are connected in series to a cell of negligible internal resistance. The emf of the cell is 5.0 V.



- (i) Explain how it may be deduced that X is an ohmic resistor.
- (ii) Suggest whether the resistance of Y increases or decreases as the voltage across it increases.
- (iii) Determine the ratio $\frac{P_X}{P_Y}$ of the power dissipated in resistor X to the power in resistor Y.

Answers

$$(a) \frac{R_x}{R_y} = \frac{\frac{\rho L}{A}}{\frac{2\rho \times 2L}{4A}} = \frac{\frac{\rho L}{\pi r^2}}{\frac{2\rho \times 2L}{\pi(2r)^2}} = \frac{\frac{\rho L}{\pi r^2}}{\frac{\rho L}{\pi r^2}} = 1.$$

(b)

(i) The top and side resistors are in series for a total of 60Ω . This and the lower one are in parallel for a total of $\frac{1}{60} + \frac{1}{20} = \frac{1}{15}$ i.e. 15Ω .

(ii) The two vertical resistors are in parallel for a total of 10Ω . This is in series with the top resistor for a total of 30Ω . This is now in parallel with the lower one for a total of $\frac{1}{30} + \frac{1}{20} = \frac{1}{12}$ i.e. 12Ω .

(c) In circuit 1 the total resistance is $\frac{3R}{2}$ and in circuit 2 it is $2R$. So the current in circuit 1 in X is

$$\frac{1}{2} \times \frac{\varepsilon}{\frac{3R}{2}} = \frac{\varepsilon}{3R} \text{ and in circuit 2 it is } \frac{\varepsilon}{2R} \text{ . Hence}$$

$$(i) \frac{P_{x1}}{P_{x2}} = \frac{R \times \left(\frac{\varepsilon}{3R}\right)^2}{R \times \left(\frac{\varepsilon}{2R}\right)^2} = \frac{4}{9} \text{ . The power in X increases in circuit 2.}$$

$$(ii) \frac{P_{y1}}{P_{y2}} = \frac{R \times \left(\frac{2\varepsilon}{3R}\right)^2}{R \times \left(\frac{\varepsilon}{2R}\right)^2} = \frac{16}{9} \text{ . The power in Y decreases in circuit 2.}$$

(d)

(i) The voltage across R is the same as that across the 10Ω resistor i.e.

$$0.80 \times 10 = 8.0 \text{ V . Hence } R = \frac{8.0}{0.20} = 40 \Omega \text{ .}$$

(ii) $V = \varepsilon - I_{\text{total}}r \Rightarrow 8.0 = 12 - 1.0r \Rightarrow r = 4.0 \Omega$.

(e)

(i) It is ohmic because the graph is a straight line through the origin.

(ii) The current increases disproportionately more than the voltage so the resistance decreases/or evaluate resistance at 2 different voltages.

(iii) X and Y are in series, so they take the same current. The sum of the voltages across X and Y must make 5.0 V and this happens for a current of 4.0 mA giving voltages 2.0 V

$$\text{across X and } 3.0 \text{ V across Y. Hence } \frac{P_x}{P_y} = \frac{V_x \times I}{V_y \times I} = \frac{2}{3} \text{ .}$$