

Quiz B11

Current and circuits

1. Electric current is established in a cylindrical metallic wire.




The current is

- A the number of electrons moving past the cross sectional area of the wire per unit time.
 - B the number of electrons moving past a point in the wire per unit time.
 - C the charge that flows through the cross sectional area of the wire per unit time.
 - D the charge in 1 cm^3 of the wire per unit time.
2. Two cylindrical wires, X and Y, have the same length. X has resistivity ρ and radius r . Y has resistivity 2ρ and radius $2r$. What is the ratio $\frac{R_X}{R_Y}$ of the resistance of X to that of Y?

- A 8 B 2 C $\frac{1}{2}$ D $\frac{1}{8}$

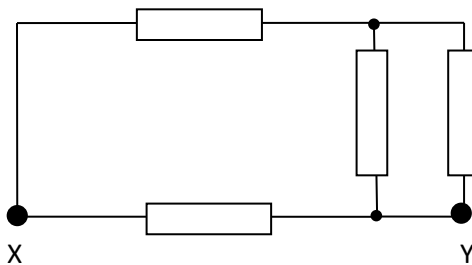3. Four resistors, each of resistance 10Ω , are connected as shown. What is the resistance between X and Y?




- A 2.5Ω B 6.0Ω C 10Ω D 30Ω

4. A cylindrical wire of resistance R is connected to a source of negligible internal resistance. The power dissipated in the wire is P . The wire is cut into two pieces of equal length. The pieces are connected in parallel to the same source. What is the total power dissipated in the circuit?

A $\frac{P}{4}$ B $\frac{P}{2}$ C $2P$ D $4P$

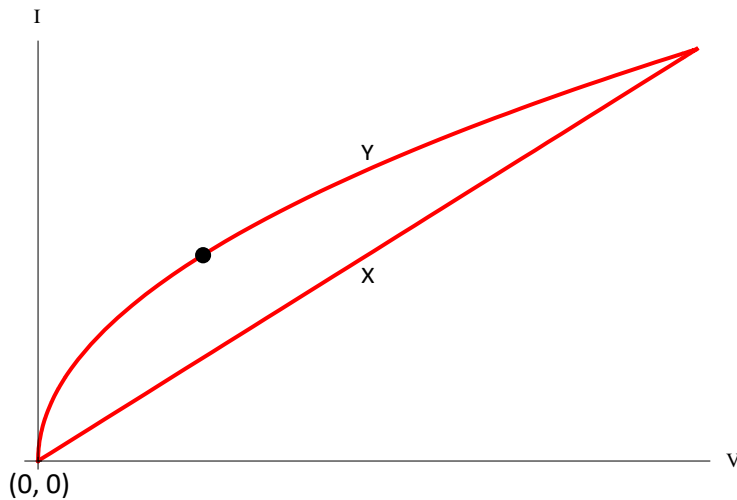5. The graph shows the I-V characteristics of two resistors X and Y. At the marked point, the tangent to the curve for Y is parallel to the graph for X.




Three statements are made about X and Y:

- I The resistance of X is constant
- II The resistance of Y increases with increasing voltage
- III Excluding the origin, X and Y have the same resistance at two different voltages


Which statements are correct?

- A I and II
- B I and III
- C II and III
- D I, II and III

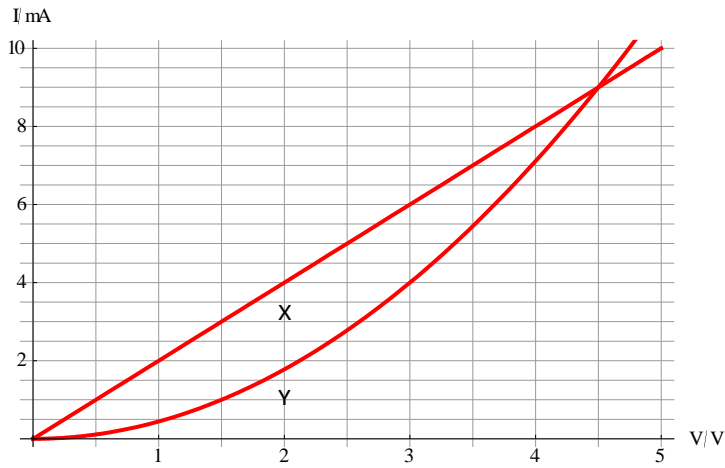6. The graph shows the I-V characteristics of two resistors X and Y.



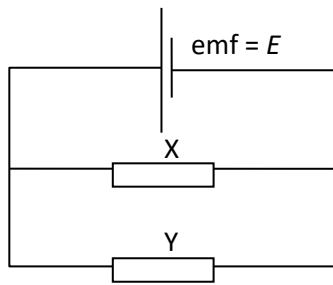
X and Y are connected to a cell of negligible internal resistance. The current leaving the cell is 10 mA.



What is the emf E of the cell?


- A 2.5 V B 3.0 V C 3.5 V D 4.5 V
7. A light bulb is rated 60 W at 220 V. What would be the power dissipated in the lamp if it is connected to a source of 110 V?
- A 15 W B 30 W C 120 W D 240 W

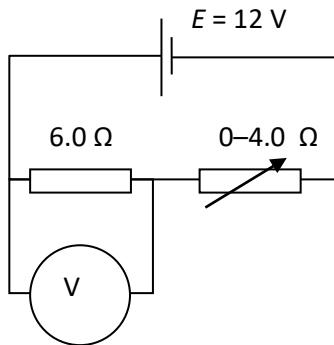8. In the circuit shown the cell has negligible internal resistance. The variable resistance can be varied from 0 to 4.0Ω .



What is the range of readings of the voltmeter as the variable resistor is varied from 4.0Ω to 0?

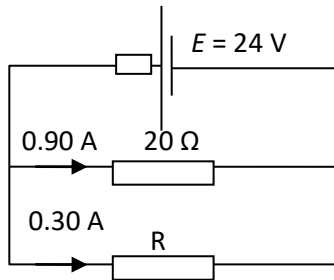
- A $0 \text{ V} - 4.8 \text{ V}$ B $0 \text{ V} - 7.2 \text{ V}$ C $4.8 \text{ V} - 12 \text{ V}$ D $7.2 \text{ V} - 12 \text{ V}$
9. A cell of emf 24 V is connected to two external resistors in parallel. The 20Ω resistor takes current 0.90 A and R takes current 0.30 A .



What is the internal resistance of the cell and what is the resistance of R?

	Internal resistance	External resistance R
A	5Ω	40Ω
B	5Ω	60Ω
C	10Ω	40Ω
D	10Ω	60Ω

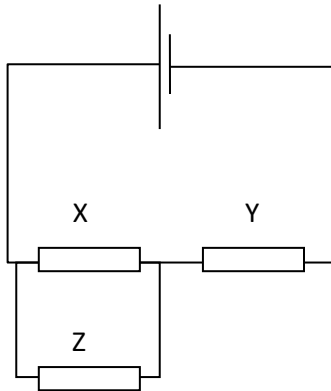10. Three identical resistors are connected as shown. The cell has no internal resistance.



Resistor Z burns out. What happens to the power dissipated in X and the power dissipated in Y?

	Power in X	Power in Y
A	decreases	decreases
B	decreases	stays the same
C	increases	decreases
D	increases	stays the same

Quiz B11 Answers	
1	C
2	B
3	B
4	D
5	A
6	B
7	A
8	D
9	B
10	C